

Two capacitors of unknown capacitances C_1 and C_2 are connected first in series and then in parallel across a battery of 100 V. If the energy stored in the two combinations is 0.045 J and 0.25 J respectively, determine the value of C_1 and C_2 . Also calculate the charge on each capacitor in parallel combination.

For series combination, energy stored

$$u_1 = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} V^2$$

$$0.045 = \frac{C_1 C_2}{2(C_1 + C_2)} (100)^2 \dots (i)$$

For parallel combination, energy stored

$$u_2 = \frac{1}{2} (C_1 + C_2) V^2$$

$$0.25 = \frac{1}{2} (C_1 + C_2) (100)^2$$

$$\therefore C_1 + C_2 = 0.5 \times 10^{-4} \dots (ii)$$

$$\text{From (i), } 0.045 = \frac{C_1 C_2}{2(0.5 \times 10^{-4})} \times 10^{-4}$$

$$C_1 C_2 = 0.045 \times 10^{-8}$$

$$\text{Now, } C_1 - C_2 = \left[(C_1 + C_2)^2 - 4C_1 C_2 \right]^{1/2}$$

$$= \left[(0.5 \times 10^{-4})^2 - 4(0.045 \times 10^{-8}) \right]^{1/2}$$

$$= \left[(0.25 \times 0.180) 10^{-8} \right]^{1/2}$$

$$C_1 - C_2 = 0.26 \times 10^{-4} \dots (iii)$$

From (ii) and (iii), we get

$$C_1 = 0.38 \times 10^{-4} F \text{ and } C_2 = 0.12 \times 10^{-4} F$$

Charges on C_1 and C_2 in parallel combination

$$q_1 = C_1 V = 0.38 \times 10^{-4} \times 100 = 0.38 \times 10^{-2} C$$

$$q_2 = C_2 V = 0.12 \times 10^{-4} \times 100 = 0.12 \times 10^{-2} C.$$

(ii) Two capacitors of different capacitances are connected first (1) in series and then (2) in parallel across a dc source of 100 V. If the total energy stored in the combination in the two cases are 40 mJ and 250 mJ respectively, find the capacitance of the capacitors.

5

OR

Question: Two capacitors of different capacitances are connected first (1) in series and then (2) in parallel across a dc source of 100 V. If the total energy stored in the combination in the two cases are 40 mJ and 250 mJ respectively, find the capacitance of the capacitors.

- Given, for series combination, energy stored is $u_s = 0.04 \text{ J}$
- Given, for parallel combination, energy stored is $u_p = 0.25 \text{ J}$
- Given the dc source voltage = $V = 100 \text{ V}$
- For series combination, energy stored is given by the formula
 - $u_s = \frac{1}{2} \left[\frac{C_1 C_2}{C_1 + C_2} \right] V^2 \Rightarrow 0.04 = \frac{1}{2} \left[\frac{C_1 C_2}{C_1 + C_2} \right] (100)^2 \Rightarrow 0.08 = \left[\frac{C_1 C_2}{C_1 + C_2} \right] 10^4 \Rightarrow 8 = \left[\frac{C_1 C_2}{C_1 + C_2} \right] 10^6$
 - $\therefore C_1 C_2 = 8[C_1 + C_2] 10^{-6} \text{ --- (1)}$

- For parallel combination, energy stored is given by
 - $u_p = \frac{1}{2} [C_1 + C_2] V^2 \Rightarrow 0.25 = \frac{1}{2} [C_1 + C_2] (100)^2 \Rightarrow 0.5 = [C_1 + C_2] (10)^4$
 - $\therefore [C_1 + C_2] = 50 \times 10^{-6} \text{ --- (2)}$

- Plug (2) in (1), we get
- $C_1 C_2 = 8[50 \times 10^{-6}] 10^{-6} = 400 \times 10^{-12} \text{ --- (3)}$
- Now, $C_1 - C_2 = \sqrt{(C_1 + C_2)^2 - 4C_1 C_2} \text{ --- (4)}$
- Plug (2) and (3) in (4), we get

- $C_1 - C_2 = \sqrt{(50 \times 10^{-6})^2 - 4 \times 400 \times 10^{-12}}$
- $C_1 - C_2 = \sqrt{2500 - 1600} \times 10^{-6} = 30 \times 10^{-6} \text{ --- (5)}$

- Solving equations (2) and (5), we get

- Adding (2) and (5), $2C_1 = 80 \times 10^{-6}$; $\therefore C_1 = 40 \mu\text{F}$
- Subtracting (2) and (5), $2C_2 = 20 \times 10^{-6}$; $\therefore C_2 = 10 \mu\text{F}$

➤ Extra 1 : Parallel combination

- Charge on each capacitor in parallel combination = $Q_1 = C_1 V = 40 \times 10^{-6} \times 100 = 4 \times 10^{-3} \text{ C} = 4 \text{ mC}$
- $Q_2 = C_2 V = 10 \times 10^{-6} \times 100 = 1 \times 10^{-3} \text{ C} = 1 \text{ mC}$
- Total charge $Q_p = Q_1 + Q_2 = 5 \text{ mC}$ (we can do this simple addition in parallel combination, not in series combination)
- Also total charge in both the capacitors in parallel combination = $Q_p = (C_1 + C_2) V = 50 \mu\text{F} \times 100 = 5 \text{ mC}$
- Verifying energy in this case:
 - $u_p = \frac{1}{2} QV = \frac{1}{2} \times 5 \text{ mC} \times 100 = 250 \text{ mJ}$ (verified)
 - $u_p = \frac{1}{2} Q^2 / C = 0.5 \times (25 \times 10^{-3})^2 / (50 \times 10^{-6}) = 0.5 \times 0.5 = 0.25 \text{ J} = 250 \text{ mJ}$ (verified)
 - $u_p = \frac{1}{2} CV^2 = \frac{1}{2} \times 50 \times 10^{-6} \times 10^4 = 25 \times 10^{-2} = 250 \text{ mJ}$ (verified)

➤ Extra 2: Series combination

- In series combination, charge on both the capacitors are same $\Rightarrow Q_1 = Q_2$
- $C_1 V_1 = C_2 V_2$ and $V_1 + V_2 = 100$; $C_1 = 40 \mu\text{F}$ and $C_2 = 10 \mu\text{F}$
- $C_1 / C_2 = 4 = V_2 / V_1$; $V_2 = 4V_1$ $\therefore V_1 = 20 \text{ V}$ and $V_2 = 80 \text{ V}$
- $Q_1 = C_1 V_1 = 40 \mu\text{F} \times 20 = 800 \mu\text{C}$
- $Q_2 = C_2 V_2 = 10 \mu\text{F} \times 80 = 800 \mu\text{C}$
- In series combination, charge on both the capacitors are same $\Rightarrow Q_1 = Q_2$
- In series combination, the charge on each capacitor = $800 \mu\text{C} = 0.8 \text{ mC}$
- Effective capacitance in series combination: $C = \frac{C_1 C_2}{C_1 + C_2} = \frac{400 \times 10^{-12}}{50 \times 10^{-6}} = 8 \mu\text{F}$
- Total charge in the series circuit = $Q_s = \left[\frac{C_1 C_2}{C_1 + C_2} \right] V = 8 \mu\text{F} \times 100 \text{ V} = 800 \mu\text{C} = 0.8 \text{ mC}$
- Note that $Q_s \neq Q_1 + Q_2$ in series combination. Since in series combination, all capacitors are charged to the same value (Q is same), $Q_s =$ charge on any one capacitor
- Verifying energy in series case:
 - $u_p = \frac{1}{2} QV = \frac{1}{2} \times 800 \mu\text{C} \times 100 = 400 \times 10^{-4} = 40 \text{ mJ}$ (verified)
 - $u_p = \frac{1}{2} Q^2 / C = [0.5 \times (0.64 \times 10^{-6})] / (8 \times 10^{-6}) = 0.5 \times 0.64 / 8 = 0.04 \text{ J} = 40 \text{ mJ}$ (verified)
 - $u_p = \frac{1}{2} CV^2 = \frac{1}{2} \times 8 \times 10^{-6} \times 10^4 = 4 \times 10^{-2} = 40 \text{ mJ}$ (verified)