

Q: Three 60 W, 120 V light bulbs are connected to 120 V supply as shown. Find (a) the voltage across each bulb

(2) total power developed in the circuit

→ 60 W bulbs have same resistances.

Total $R_{\text{eq}} = R + R/2$



$R_{\text{total}} = R + R/2 = \frac{3}{2} R$

$I = \frac{120}{\frac{3}{2} R} = \frac{80}{R}$

$\therefore V_A = IR = \frac{80}{R} \cdot R = 80 \text{ V}$

$V_B = I/2 \cdot R = \frac{I}{2} \times R = \frac{I}{2} \times \frac{R}{2} = \frac{80}{R} \times \frac{R}{2} = 40 \text{ V}$

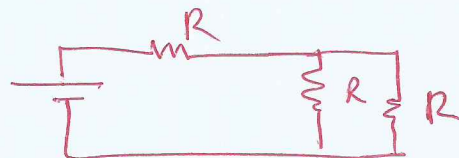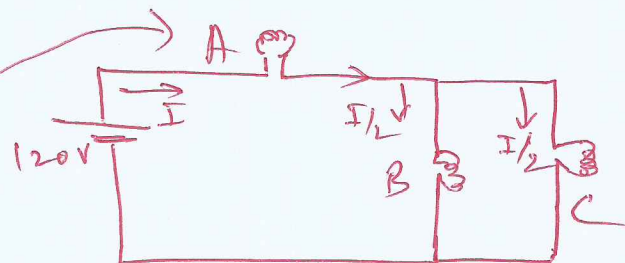$V_C = I/2 \cdot R = \frac{I}{2} \times R = \frac{I}{2} \times \frac{R}{2} = \frac{80}{R} \times \frac{R}{2} = 40 \text{ V}$



→ (b) Total power

B & C are in parallel, so total power = $P_B + P_C = 60 + 60 = 120 \text{ W}$


A is in series with B || C (60 W || 120 W)

$\therefore \frac{60 \times 120}{60 + 120} = \frac{60 \times 120}{180} = 40 \text{ W}$

Q:

50 W bulb (max rating 200 V)

100 W bulb (max. vol. rating = 200 V)

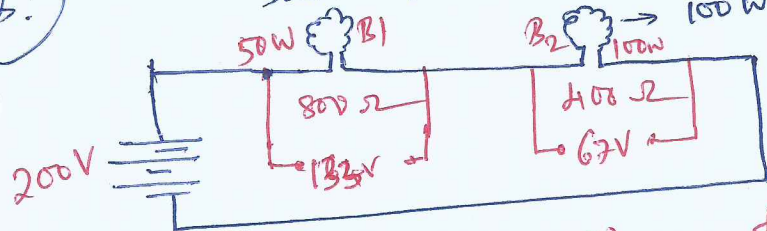

Which bulb glows more
which bulb is brighter?
 B_1 or B_2 ?

- Calculate R of each bulb $R = \frac{V^2}{P}$

bulb 1 $\rightarrow \frac{200^2}{50} = 800 \Omega$
bulb 2 $\rightarrow \frac{200^2}{100} = 400 \Omega$


→ Current in circuit $I = \frac{200}{800 + 400} = \frac{200}{1200} = \frac{1}{6} \text{ A}$

→ Voltage across each bulb
bulb 1 $\rightarrow V_{\text{bulb1}} = IR = \frac{1}{6} \times 800 = 133 \text{ V}$
bulb 2 $\rightarrow V_{\text{bulb2}} = IR = \frac{1}{6} \times 400 = 67 \text{ V}$

→ 50 W bulb glows brighter since $P \propto V \rightarrow 50 \text{ W}$ will consume more power than 100 W bulb.

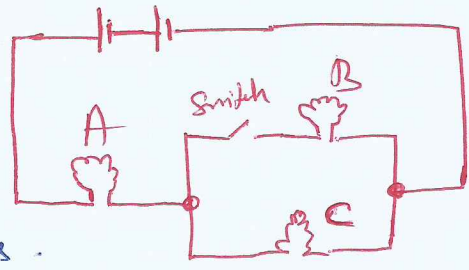Q: 3 Bulbs A, B and C are connected as shown. What changes occur in brightness of the bulbs when switch is closed?

- ✓ (a) Brightness of A increases, but that of C decreases
- (b) — " — A remains same but of C — "
- (c) — " — of both A and C decreases
- (d) — " — of A increases, but that of C remains same.




→ When switch is open, A and C are glowing depending on their power ratings.

→ When switch is closed, effective resistance in B & C loop decreases \Rightarrow overall resistance decreases \Rightarrow this will increase the current \Rightarrow A gets more current \Rightarrow and since brightness of bulb $\propto I^2$, brightness of A increases.

→ Now the current is shared betⁿ B and C, therefore, the brightness of the bulb C decreases.

Q: A 100W bulb B_1 and two 60W bulbs B_2 and B_3 are connected to a 250V source as shown. Now W_1 , W_2 and W_3 are the output powers of the bulbs B_1 , B_2 and B_3 respectively, then

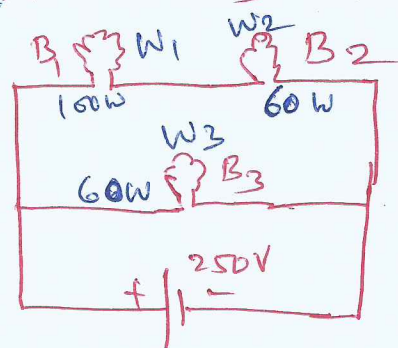- (a) $W_1 > W_2 = W_3$
- (b) $W_1 > W_2 > W_3$
- (c) $W_1 < W_2 = W_3$
- ✓ (d) $W_1 < W_2 < W_3$



→ Voltage across B_3 is greatest, hence B_3 will show maximum brightness.

→ B_1 and B_2 are in series \Rightarrow hence the bulb of lesser voltage will glow more ~~than~~ bright (than B_1)

Hence $W_2 > W_1$ and also from above $W_3 > W_2$ and $W_3 > W_1$

$\therefore W_3 > W_2 > W_1$ or $W_1 < W_2 < W_3$

Q: The supply voltage to room is 120V. The resistance of the connecting wires is $6\ \Omega$. A 60W bulb is already switched on. What is the decrease of the voltage across the bulb, when a 240W heater is switched on in parallel to bulb.

Given $V = 120V$, $P = 60W$
Connecting wire resistance $= 6\ \Omega$

$$R_{\text{bulb}} = \frac{V^2}{P} = \frac{120^2}{60} = 240\ \Omega$$

(Since $P = V^2/R$) $\therefore V_{\text{bulb}} =$ Voltage across bulb
 $V_{\text{bulb}} =$

$$\therefore R_{\text{eq}} = 240 + 6 = 246\ \Omega$$

$$\text{Vol. across bulb} = V_B = \frac{120}{246} \times 240$$

$$V_B = 117.07V$$

Now heater is connected (as shown in fig 2)

$$R_{\text{heater}} = \frac{V^2}{P} = \frac{120^2}{240} = 60\ \Omega$$

$$\therefore \text{Equivalent resistance of circuit} = 6 + \frac{240 \times 60}{240 + 60} = 6 + \frac{240 \times 60}{300} = 54\ \Omega$$

$$\therefore \text{Voltage across bulb} = V_B' = \frac{120}{54} \times 48 = 106.66V$$

$$\text{Change in voltage} = 117.07 - 106.66 = 10.41V$$

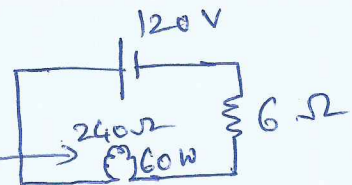


fig 1


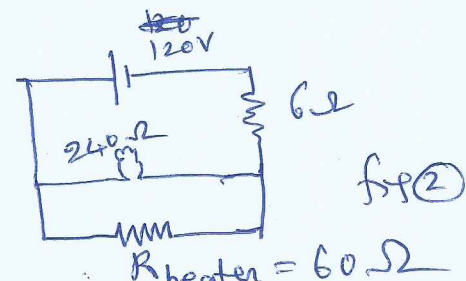


fig 2

In the given problem (see right), all resistors are equal, say R ohms.

The equivalent circuit is

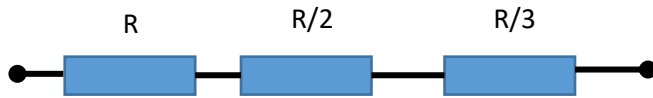

The equivalent resistance = $R + R/2 + R/3$



$$= R \left(1 + \frac{1}{2} + \frac{1}{3} \right) = R \left(\frac{3}{2} + \frac{1}{3} \right)$$

$$= R \left\{ \frac{9+2}{6} \right\} = R \left(\frac{11}{6} \right)$$


Given equivalent resistance = $66 \text{ k}\Omega$

Therefore, $R \left(\frac{11}{6} \right) = 66 \text{ k}\Omega$

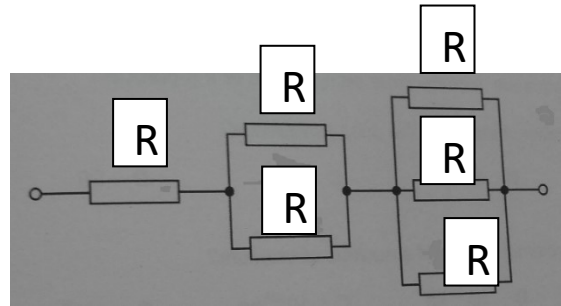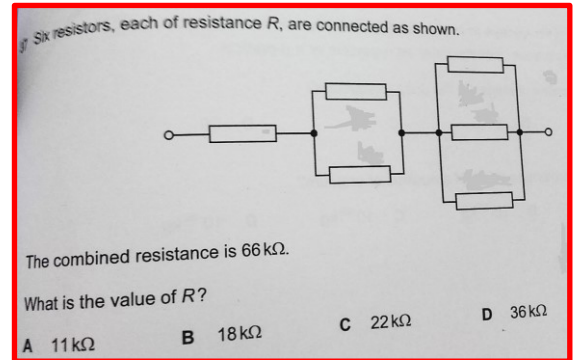So, $R = (66 \times 6)/11 = 6 \times 6 = 36 \text{ k}\Omega$; Answer is [D]



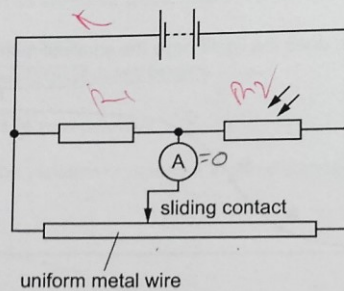36 In the potentiometer circuit shown, the reading on the ammeter is zero.



The light-dependent resistor (LDR) is then covered up and the ammeter gives a non-zero reading.

Which change could return the ammeter reading to zero?

- A Decrease the supply voltage.
- B Increase the supply voltage.
- ☒ C Move the sliding contact to the left.
- D Move the sliding contact to the right.

- We know that the resistance of a photoresistor decreases with increasing incident light intensity.
- The equivalent circuit portion is a Wheatstone bridge
- $R_1/R_2 = R_3/R_4$
- When LDR is covered, R_2 value increases, hence R_1/R_2 decreases
- $\therefore R_3/R_4$ should also decrease to get null reading
- $\therefore R_3$ to be made lower value or R_4 to be made a bigger value
- For R_3 to become smaller value and R_4 to increase, the sliding contact has to be moved towards left so that R_3 decreases and R_4 increases and ratio R_3/R_4 remains constant and we get null point (no current in the ammeter)

➤ **Answer is [C]**

